


Assignment #6 E & CE 223

E&CE 223
Assignment 6 - Solutions


1: Mano 6.1 and 6.2

Mano 6.1


See Notes page 187

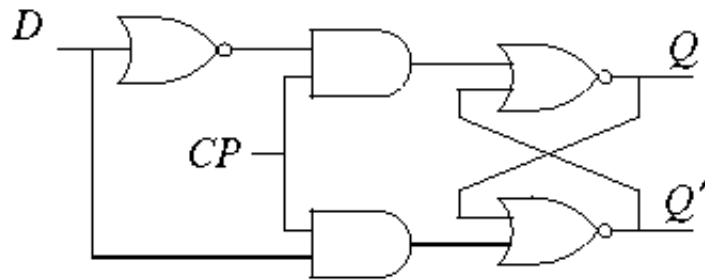

Mano 6.2

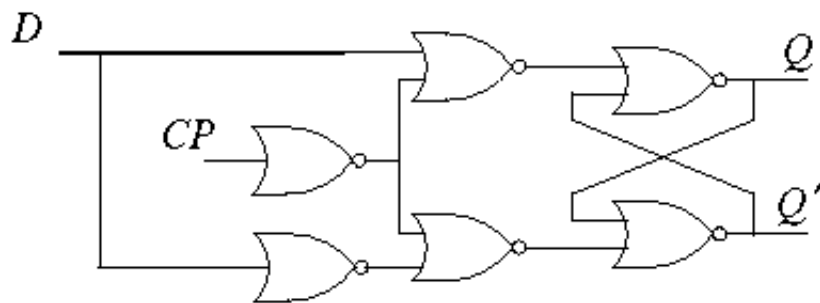

2: Mano 6.4

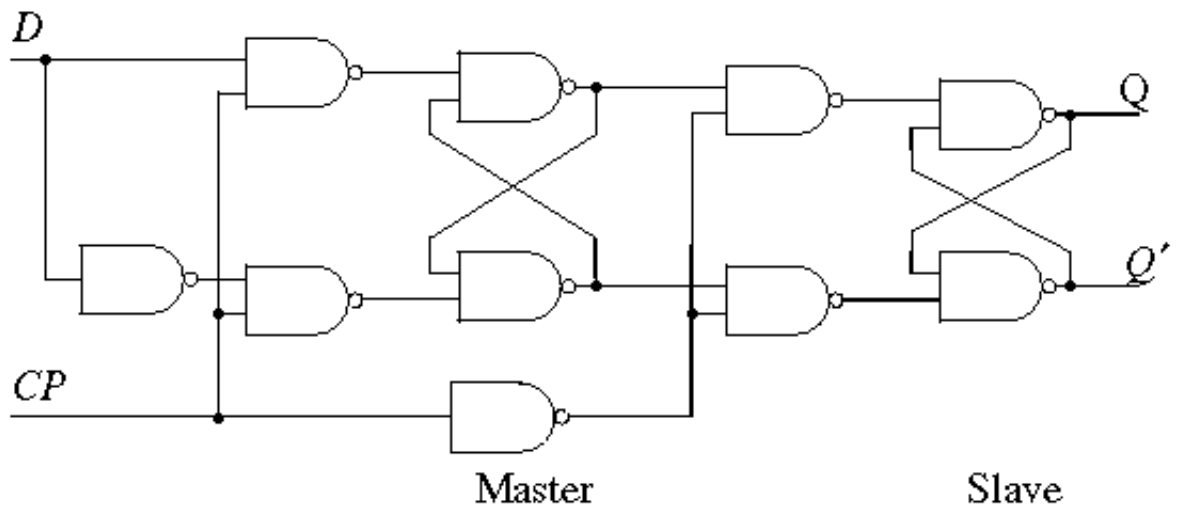


3: Mano 6.9

$$T_A = A + B$$

$$T_B = A' + B$$


present state AB	T_A	T_B	next state AB
00	0	1	01
01	1	1	10
10	1	0	00
11	1	1	00

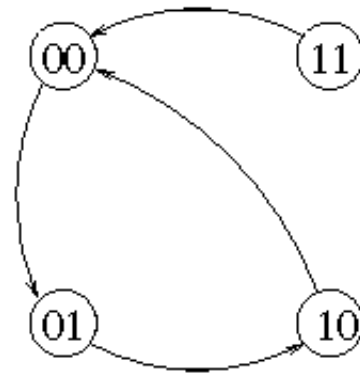

Counter with the sequence 00, 01, 10, 00 etc.

4: Mano 6.12

(a)

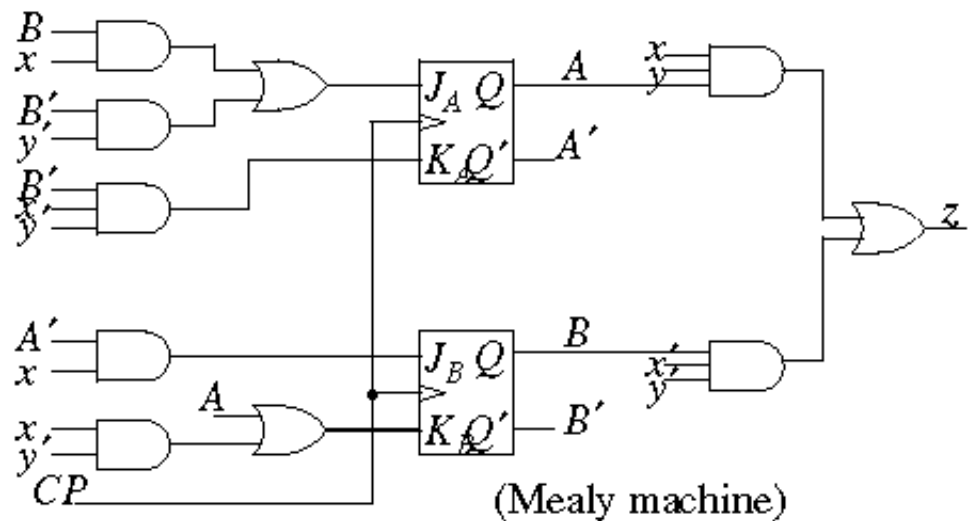

(b)

present state		inputs		FF inputs				next state		output
A	B	x	y	J_A	K_A	J_B	K_B	A	B	z
0	0	0	0	1	0	0	0	1	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	1	1	1	1	1	0
0	0	1	1	0	0	1	0	0	1	0
0	1	0	0	0	0	0	0	0	1	1
0	1	0	1	0	0	0	0	0	1	0
0	1	1	0	1	0	1	1	1	0	0
0	1	1	1	1	0	1	0	1	1	0
1	0	0	0	1	0	0	1	1	0	0
1	0	0	1	0	0	0	1	1	0	0
1	0	1	0	1	1	0	1	0	0	0
1	0	1	1	0	0	0	1	1	0	1
1	1	0	0	0	0	0	1	1	0	1
1	1	0	1	0	0	0	1	1	0	0
1	1	1	0	1	0	0	1	1	0	0
1	1	1	1	1	0	0	1	1	0	1

(c)

AB \ xy	00	01	11	10
00	1			1
01			1	1
11	1	1	1	1
10	1	1	1	

A_{z+1}

AB \ xy	00	01	11	10
00			1	1
01	1	1	1	
11				
10				

B_{z+1}

$$A_{z+1} = Ax' + Bx + Ay + A'B'y'$$

$$B_{z+1} = A'B'x + A'Bx' + A'By$$


5: Mano 6.21

Binary up-down counter with enable input E

present state		inputs		next state		FF transitions	
A	B	E	x	A	B	A	B
0	0	0	0	0	0	ϕ	ϕ
0	0	0	1	0	0	ϕ	ϕ
0	0	1	0	1	1	α	α
0	0	1	1	0	1	ϕ	α
0	1	0	0	0	1	ϕ	I
0	1	0	1	0	1	ϕ	I
0	1	1	0	0	0	ϕ	β
0	1	1	1	1	0	α	β
1	0	0	0	1	0	I	ϕ
1	0	0	1	1	0	I	ϕ
1	0	1	0	0	1	β	α
1	0	1	1	1	1	I	α
1	1	0	0	1	1	I	I
1	1	0	1	1	1	I	I
1	1	1	0	1	0	I	β
1	1	1	1	0	0	β	β

The transitions in the above table were derived from the current state and next state using the relations:

Q_n	Q_{n+1}	transition
0	0	ϕ
0	1	α
1	0	β
1	1	I

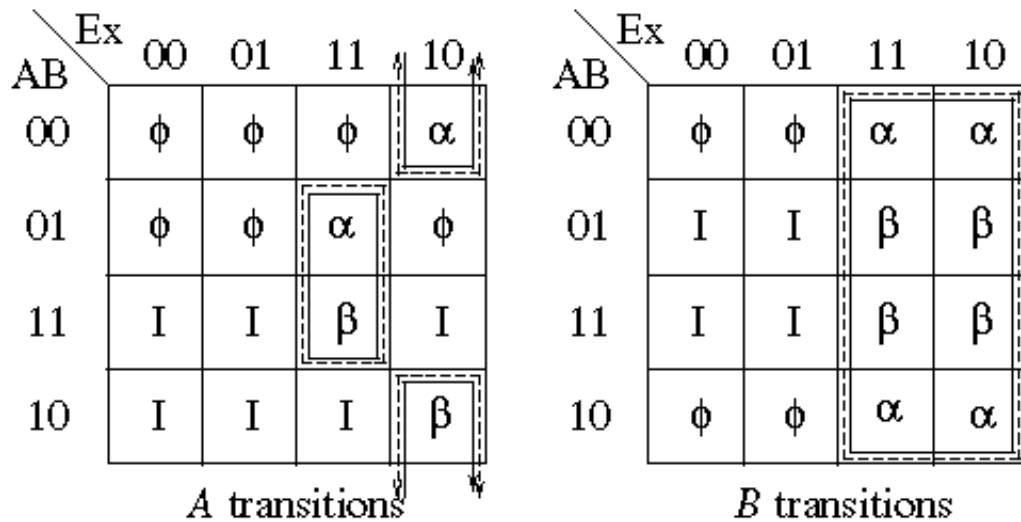

Recall that:

- J must include α , may include β, I
- K must include β , may include α, ϕ

This leads to groupings shown on maps:

- solid - J
- dashed - K

$$J_A = K_A = (Bx+B'x')E \qquad J_B = K_B = E$$

Aside:

From the transition tables it is obvious that JK gives a simpler circuit than SR does. Recall that:

- S must include α , may include I
- R must include β , may include ϕ

$$S_A = (Bx+B'x')EA' \qquad S_B = EB$$

$$R_A = (Bx+B'x')EA \qquad R_B = EB'$$

6: Mano 6.22

present state			next state						output	
A	B	C	x=0			x=1			x=0	x=1
A	B	C	A	B	C	A	B	C		
0	0	0	0	1	1	1	0	0	0	1
0	0	1	0	0	1	1	0	0	0	1
0	1	0	0	1	0	0	0	0	0	1
0	1	1	0	0	1	0	1	0	0	1
1	0	0	0	1	0	0	1	1	0	0
1	0	1	-	-	-	-	-	-	-	-
1	1	0	-	-	-	-	-	-	-	-
1	1	1	-	-	-	-	-	-	-	-

Karnaugh Maps:

AB	Cx				AB	Cx				AB	Cx			
	00	01	11	10		00	01	11	10		00	01	11	10
00	0	1	1	0	00	1	0	0	0	00	1	0	0	1
01	0	0	0	0	01	1	0	1	0	01	0	0	0	1
11	-	-	-	-	11	-	-	-	-	11	-	-	-	-
10	0	0	-	-	10	1	1	-	-	10	0	1	-	-
	A_{n+1}					B_{n+1}					C_{n+1}			

The D flip-flop excitation can be derived directly from the K-map. We will generate the transition maps and do D, SR, JK and T from that common base.

Transition Maps:

	Cx					Cx					Cx			
AB	00	01	11	10	AB	00	01	11	10	AB	00	01	11	10
00	ϕ	α	α	ϕ	00	α	ϕ	ϕ	ϕ	00	α	ϕ	β	I
01	ϕ	ϕ	ϕ	ϕ	01	I	β	I	β	01	ϕ	ϕ	β	I
11	-	-	-	-	11	-	-	-	-	11	-	-	-	-
10	β	β	-	-	10	α	α	-	-	10	ϕ	α	-	-
	A					B					C			

	"Set Inputs"		"Reset Inputs"	
D	$D = (\alpha, I)$	$X = (-)$		
SR	$S = (\alpha)$	$X = (-, I)$	$R = (\beta)$	$X = (-, \phi)$
JK	$J = (\alpha)$	$X = (-, I, \beta)$	$K = (\beta)$	$X = (-, \phi, \alpha)$
T	$T = (\alpha, \beta)$	$X = (-)$		

D flip-flops:

	Cx					Cx					Cx			
AB	00	01	11	10	AB	00	01	11	10	AB	00	01	11	10
00	ϕ	α	α	ϕ	00	α	ϕ	ϕ	ϕ	00	α	ϕ	β	I
01	ϕ	ϕ	ϕ	ϕ	01	I	β	I	β	01	ϕ	ϕ	β	I
11	-	-	-	-	11	-	-	-	-	11	-	-	-	-
10	β	β	-	-	10	α	α	-	-	10	ϕ	α	-	-
	A					B					C			

$$D_A = A'B'x \quad D_B = C'x' + A + BCx \quad D_C = A'B'x' + Ax + Cx'$$

Note these equations could have been developed directly from the K-map.

Self correcting?

Yes. $D_A=0$ in all invalid states, causing A to be reset to a valid state.

$$J_A = B'x$$

$$K_A = 1$$

$$J_B = C'x' + A$$

$$K_B = C'x + Cx'$$

$$J_C = A'B'x' + Ax$$

$$K_C = x$$

Self correcting?

Yes. $K_A=1$. If any of the invalid states are entered, A is reset or toggled to a valid state.

T flip-flops:

		Cx			
		00	01	11	10
AB	00	ϕ	α	α	ϕ
	01	ϕ	ϕ	ϕ	ϕ
	11	-	-	-	-
	10	β	β	-	-
		A			

		Cx			
		00	01	11	10
AB	00	α	ϕ	ϕ	ϕ
	01	I	β	I	β
	11	-	-	-	-
	10	α	α	-	-
		B			

		Cx			
		00	01	11	10
AB	00	α	ϕ	β	I
	01	ϕ	ϕ	β	I
	11	-	-	-	-
	10	ϕ	α	-	-
		C			

$$T_A = B'x + A \quad T_B = B'C'x' + A + BCx' \quad T_C = A'B'C'x' + Ax + Cx$$

Self correcting?

Yes. $T_A = \dots + A$. In all the invalid states this causes A to be toggled, leading to a valid state.

In all cases the output is:

		Cx			
		00	01	11	10
AB	00		I	I	
	01		I	I	
	11	X	X	X	X
	10			X	X
		y			

$$y = A'x$$

7: Mano 6.25 (a) and (b)

(a) JK flip-flops, count sequence 0,1,2,3,4,5,6

present state			next state			F/F transition		
y_3	y_2	y_1	y_3	y_2	y_1	y_3	y_2	y_1
0	0	0	0	0	1	ϕ	ϕ	α
0	0	1	0	1	0	ϕ	α	β
0	1	0	0	1	1	ϕ	I	α
0	1	1	1	0	0	α	β	β
1	0	0	1	0	1	I	ϕ	α
1	0	1	1	1	0	I	α	β
1	1	0	0	0	0	β	β	ϕ
1	1	1	-	-	-	-	-	-

Transition Maps:

	y_1	0	1
y_3y_2	00	ϕ	ϕ
	01	ϕ	α
	11	β	-
	10	I	I

y_3 transitions

	y_1	0	1
y_3y_2	00	ϕ	α
	01	I	β
	11	β	-
	10	ϕ	α

y_2 transitions

	y_1	0	1
y_3y_2	00	α	β
	01	α	β
	11	ϕ	-
	10	α	β

y_1 transitions

$$J_3 = y_2y_1$$

$$J_2 = y_1$$

$$J_1 = y_1' + y_2'$$

$$K_3 = y_2$$

$$K_2 = y_3 + y_1$$

$$K_1 = 1$$

Check of unused states:

(111) \Rightarrow (000) OK - no trap

(b) D flip-flops, count sequence 0,1,2,4,6

Do not need transition table - just use k-map of next states

present state			next state		
y_3	y_2	y_1	y_3	y_2	y_1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	-	-	-
1	0	0	1	1	0
1	0	1	-	-	-
1	1	0	0	0	0
1	1	1	-	-	-

$y_3y_2 \backslash y_1$	0	1
00	0	0
01	1	-
11	0	-
10	1	-

$y_3(n+1)$

$y_3y_2 \backslash y_1$	0	1
00	0	1
01	0	-
11	0	-
10	1	-

$y_2(n+1)$

$y_3y_2 \backslash y_1$	0	1
00	1	0
01	0	-
11	0	-
10	0	-

$y_1(n+1)$

$$D_3 = y_3 \oplus y_2$$

$$D_2 = y_1 + y_3 y_1'$$

$$D_1 = y_3' y_2' y_1'$$

Self correcting:

(011) \Rightarrow (110) OK, no trap

(101) \Rightarrow (110) OK, no trap

(111) \Rightarrow (010) OK, no trap